

## CLASS7

## SCIENCE

### CHAPTER –ELECTRICITY AND CIRCUITS

**Q1:** Differentiate between electric current and electric circuit.

**Q2:** Explain the formation and uses of battery.


**Q3:** Explain the function of cell in a circuit.

**Q4:** An electrician is carrying out some repairs in a building. He wants to replace a fuse by a piece of wire. Would you agree with the electrician? Give reasons for your response.

**Q5:** How fuses are useful?

**Q6:** Can we use an electromagnet separating plastic bags from a garbage heap? Explain.

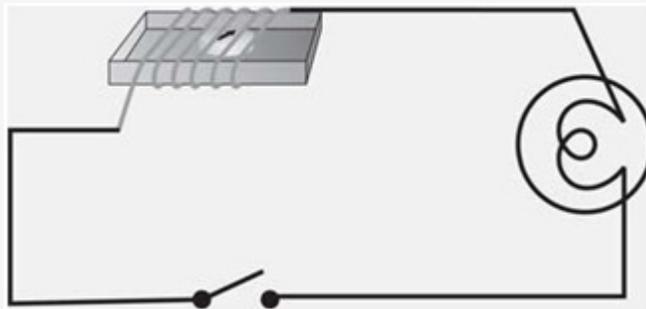**Q7:** Look at the figure given below and answer whether the compass needle will show deflection or not when the switch in the circuit shown is closed?



**Q8:** When the current is switched on through a wire, a compass needle kept nearby gets deflected from its north-south position. Explain.

**Q9:** Write short notes on heating effects of electric current.

**Q10:** Write short notes on magnetic effects of electric current

**Q11:** What are filaments of a bulb and a heater made up of?

**Q12:** State the factors on which amount of heat produced depends?

**Q13:** Why does electric current show magnetic effect?

**Q14:** Why are fuse wire not used in circuit containing electric cell?

**Q15:** Why does electric current show heating effect?

**Q16:** What is magnetic field?

**Q17:** Write short notes on Short Circuiting.

**Q18:** Write short notes on Overloading.

**Q19:** Mention the differences between an electromagnet and a permanent magnet.

**Fill in the blanks:**

1. An electric circuit is a closed path in which ..... flows.
2. A solenoid carrying current behaves like a .....
3. The space around a magnet where its influence can be experienced is called the .....
4. The combination of two or more cells is called a .....
5. When current is switched 'on' in a room heater, it gets .....
6. The safely device based on the heating effect of electric current is called a .....

**Write True (T) or False (F) against the following statements in the given brackets:**

1. Current flows through a circuit when it is open. ( )
2. Electric bell is based on the heating effect of current. ( )
3. An electric bell has an electromagnet. ( )
4. To make a battery of two cells, the negative terminal of one cell is connected to the negative terminal of the other cell. ( )
5. When the electric current through the fuse exceeds a certain limit, the fuse wire melts and breaks. ( )
6. The magnetic strength in a conductor decreases with the increase in current. ( )

**Question Answer**

7. Air is not filled in electric bulbs. Why? Justify your answer.

8. Rahul was carrying out repairs in his house. He wishes to replace a fuse by a piece of wire. Would you agree? Give reason for your response.

9. In the devices like electric heater, electric geyser, electric bulb-the heating effect of current can be put to good use. Can you think of the situations where this effect results in wastage of energy?